

## 5<sup>η</sup> Εργαστηριακή Άσκηση

### ΓΙΑ ΣΧΕΔΙΑΣΗ ΜΙΑΣ ΑΠΛΗΣ ΑΡΙΘΜΟΜΗΧΑΝΗΣ

Ομάδα LAB20332061

ΛΑΜΠΡΙΑΝΗ ΤΣΑΠΑΝΟΥ 2014030015
ΑΝΑΣΤΑΣΙΟΣ ΜΠΟΚΑΛΙΔΗΣ 2014030069

#### Σκοπός εργαστηριακής άσκησης

Σκοπός του 5<sup>ου</sup> εργαστηρίου είναι να εξελίξουμε τα 2 προηγούμενα εργαστήρια. Για την ακρίβεια σε αυτό το εργαστήριο πρέπει να υλοποιήσουμε τις λογικές πράξεις :

- Πρόσθεση αριθμών 2's complement ( $TOS + "TOS-1"$ )
- Αφαίρεση αριθμών 2's complement ( $TOS - "TOS-1"$ )
- Μοναδιαία αφαίρεση 2's complement (unary subtraction, το TOS γίνεται -TOS)
- Εναλλαγή TOS με TOS-1 (γνωστή και σαν  $X <> Y$ )

Φυσικά για να λειτουργήσουν οι παραπάνω πράξεις, πρέπει να λειτουργούν σωστά οι προηγούμενες λειτουργίες που υλοποιήσαμε στα εργαστήρια 3,4.

#### Προεργασία – Περιγραφή

Το κύκλωμα μας σε αυτό το εργαστήριο αποτελείται από τα παρακάτω υποκυκλώματα :

- Την στοίβα (**Stack**) με μνήμη πλάτους 8-bit και μήκους 32-bit, η οποία μπορεί να αποθηκεύσει μέχρι και 31 στοιχεία. Υλοποιήθηκε αυτόματα μέσω του Xilinx Core Generator
- Τους 2 **5-bit Counter** (μετρητή) όπου χρειάζεται για το TOS και το TOS-1 (έναν counter για το καθένα). Τον υλοποιήσαμε σε structural μορφή. Για την υλοποίηση του counter χρησιμοποιήθηκαν **MUX 4:1** οι οποίες υλοποιήθηκαν μέσω της χρήσης **MUX 2:1**.
- Τον συγκριτή (**Comparator**). Οι 2 comparator του κυκλώματός μας έλεγχαν αν η στοίβα μας βρισκόταν σε κατάσταση Empty ή Full.
- Την **FSM2** όπου διαβάζει το input του BTN2 (mode) και αλλάζει το mode που βρισκόμαστε και έχει ως έξοδο 00 για mode\_0, 01 για mode\_1 και 10 για mode\_2.
- Την **FSM1** όπου σε αυτήν περιέχουμε όλες τις καταστάσεις για όλες τις λειτουργίες που χρειάζεται σε αυτό το εργαστήριο. Στην ουσία είναι η FSM1 που χρησιμοποιήσαμε στα προηγούμενα εργαστήρια, απλώς προσθέσαμε κάποιες έξτρα καταστάσεις. Για παράδειγμα προσθέσαμε καταστάσεις όπου ελέγχουν πότε πρέπει να ενεργοποιούνται οι καταχωρητές που αποθηκεύουν τους αριθμούς που


χρειάζονται για τις λογικές πράξεις, καθώς επίσης και το πότε θα πρέπει να κάνει pop και push η στοίβα μας πριν ή μετά την επιτυχή ή μη επιτυχή πράξη μας.

- Τους 3 **Registers** μας όπου σε αυτούς αποθηκεύουμε τα στοιχεία μας από το TOS και το TOS-1 της στοίβας μας και το αποτέλεσμα του Αθροιστή/Αφαιρετή. Επίσης τον ένα register τον χρησιμοποιούμε διαφορετικά στις λειτουργίες UnarySub και TOS<>TOS-1 καθώς πρέπει να τον αρχικοποιούμε στο μηδέν.
- Τον **Αθροιστή/Αφαιρετή** μας ο οποίος κάνει τις πράξεις που χρειάζονται σε αυτό το εργαστήριο. Σε αυτόν προσθέσαμε και την λειτουργία που χρειάζεται στις αφαιρέσεις, δηλαδή την λειτουργία όπου μετατρέπει τον δεύτερο αριθμό στον αντίστοιχο αρνητικό του. Στην ουσία αυτή η λειτουργία είναι αυτή η οποία καθορίζει για τον αν είναι το κύκλωμα αυτό Αθροιστής ή Αφαιρετής.
- Την λειτουργία όπου ελέγχει αν μετά τις πράξεις υπάρχει overflow στο αποτέλεσμα σύμφωνα με την περιγραφή που μας δώσατε στο αντίστοιχο φροντιστήριο.
- Το entity του SSD όπου αποτελείται από: Το control\_path: ssd\_counter, ssd\_comparator, ssd\_fsm To data\_path: ssd\_encoder, ssd\_decoder, ssd\_mux


Η συνολική σύνδεση των προηγούμενων υποκυκλωμάτων έγινε στον κώδικα του Top Level.

Παρακάτω παρατίθενται τα διαγράμματα των κυκλωμάτων που υλοποιήθηκαν:


### Fsm1

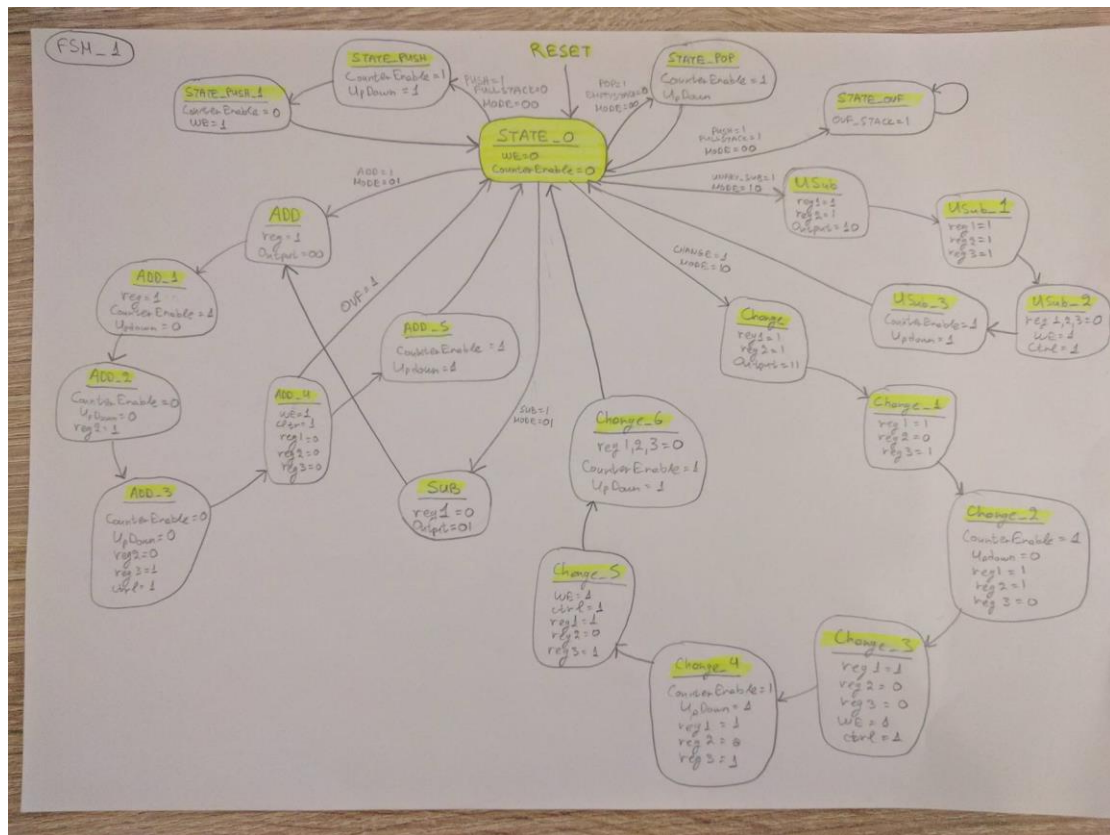

## Fsm2

 


## Top Level

 


# Κυματομορφές-Προσομοίωση


## Add

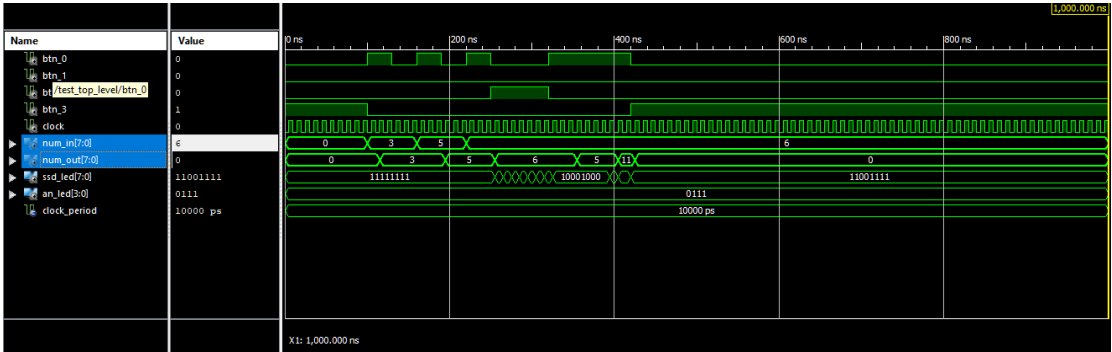


## Sub

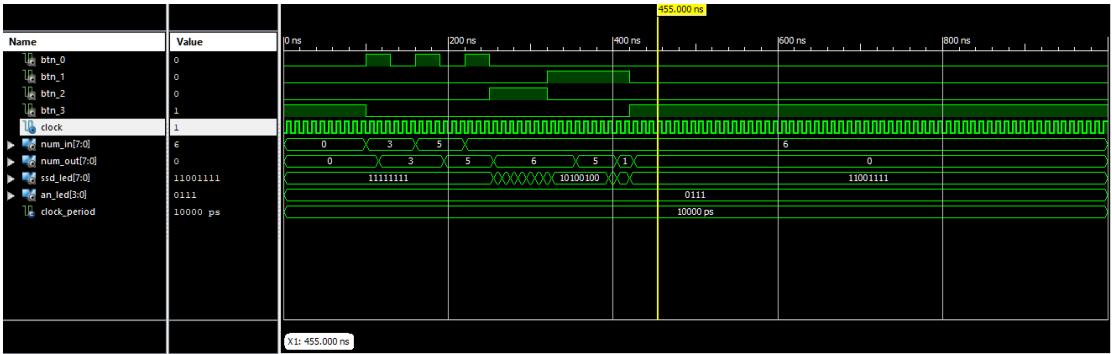

U Sub

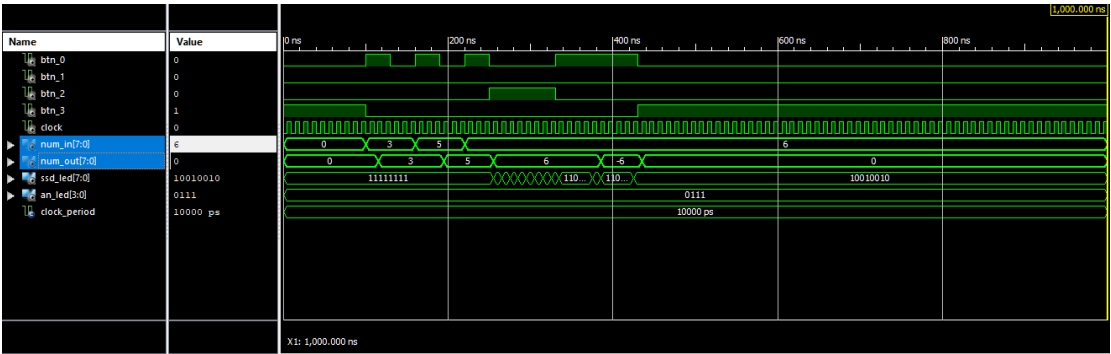

TOS <> TOS-1

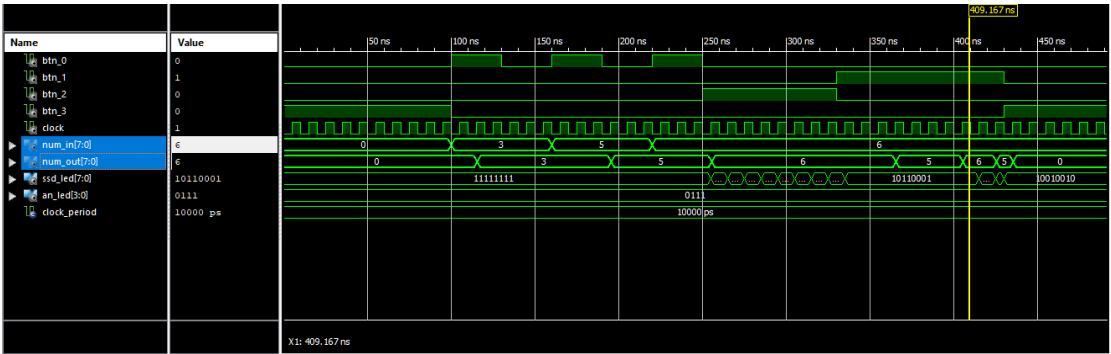

## Κώδικας

### CLA

```
32 entity CLA is
33     Port ( P : in  STD_LOGIC_VECTOR (3 downto 0);
34           G : in  STD_LOGIC_VECTOR (3 downto 0);
35           Cin : in  STD_LOGIC;
36           C : out STD_LOGIC_VECTOR (2 downto 0);
37           Cout : out STD_LOGIC);
38 end CLA;
39
40 architecture Structural of CLA is
41 begin
42     C(0) <= G(0) OR (P(0) AND Cin);
43     C(1) <= G(1) OR (P(1) AND G(0)) OR (P(1) AND P(0) AND Cin);
44     C(2) <= G(2) OR (P(2) AND G(1)) OR (P(2) AND P(1) AND G(0)) OR (P(2) AND P(1) AND P(0) AND Cin);
45     Cout <= G(3) OR (P(3) AND G(2)) OR (P(3) AND P(2) AND G(1)) OR (P(3) AND P(2) AND P(1) AND P(0) AND Cin);
46 end Structural;
```

### CPG

```
32 entity CPG is
33     Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
34           B : in  STD_LOGIC_VECTOR (3 downto 0);
35           P : out STD_LOGIC_VECTOR (3 downto 0);
36           G : out STD_LOGIC_VECTOR (3 downto 0));
37 end CPG;
38
39 architecture Structural of CPG is
40 begin
41     P(0) <= A(0) XOR B(0);
42     P(1) <= A(1) XOR B(1);
43     P(2) <= A(2) XOR B(2);
44     P(3) <= A(3) XOR B(3);
45
46     G(0) <= A(0) AND B(0);
47     G(1) <= A(1) AND B(1);
48     G(2) <= A(2) AND B(2);
49     G(3) <= A(3) AND B(3);
50 end Structural;
```

### SUM

```
32 entity SUM is
33     Port ( P : in  STD_LOGIC_VECTOR (3 downto 0);
34           C : in  STD_LOGIC_VECTOR (2 downto 0);
35           Cin : in  STD_LOGIC;
36           S : out STD_LOGIC_VECTOR (3 downto 0));
37 end SUM;
38
39 architecture Structural of SUM is
40 begin
41     S(0) <= P(0) XOR Cin;
42     S(1) <= P(1) XOR C(0);
43     S(2) <= P(2) XOR C(1);
44     S(3) <= P(3) XOR C(2);
45 end Structural;
```

## CLA\_4\_bit\_Adder

```
31
32 entity CLA_4bit_ADDER is
33     Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
34           B : in  STD_LOGIC_VECTOR (3 downto 0);
35           Cin : in  STD_LOGIC;
36           S : out  STD_LOGIC_VECTOR (3 downto 0);
37           C3 : out  STD_LOGIC);
38 end CLA_4bit_ADDER;
39
40 architecture Structural of CLA_4bit_ADDER is
41
42     component CPG
43     Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
44           B : in  STD_LOGIC_VECTOR (3 downto 0);
45           P : out  STD_LOGIC_VECTOR (3 downto 0);
46           G : out  STD_LOGIC_VECTOR (3 downto 0));
47     end component;
48
49     component CLA
50     Port ( P : in  STD_LOGIC_VECTOR (3 downto 0);
51           G : in  STD_LOGIC_VECTOR (3 downto 0);
52           Cin : in  STD_LOGIC;
53           C : out  STD_LOGIC_VECTOR (2 downto 0);
54           Cout : out  STD_LOGIC);
55     end component;
56
57     component SUM
58     Port ( P : in  STD_LOGIC_VECTOR (3 downto 0);
59           C : in  STD_LOGIC_VECTOR (2 downto 0);
60           Cin : in  STD_LOGIC;
61           S : out  STD_LOGIC_VECTOR (3 downto 0));
62     end component;
63
64     signal G_signal:std_logic_vector(3 downto 0);
65     signal P_signal:std_logic_vector(3 downto 0);
66     signal C_signal:std_logic_vector(2 downto 0);
67
68     begin
69     CPG_unit: CPG
70     port map( A=>A,
71             B=>B,
72             P=>P_signal,
73             G=>G_signal);
74
75     CLA_unit: CLA
76     port map( P=>P_signal,
77             G=>G_signal,
78             Cin=>Cin,
79             C=>C_signal,
80             Cout=>C3);
81
82     SUM_unit: SUM
83     port map( P=>P_signal,
84             C=>C_signal,
85             Cin=>Cin,
86             S=>S);
87
88 end Structural;
```

Οι παραπάνω εικόνες κώδικα είναι τα υποκυκλώματα του CLA που χρειάζονται για την υλοποίηση του σε structural δομή όπως μας ζητήθηκε τώρα και στο 2<sup>ο</sup> εργαστήριο. Για αυτό το εργαστήριο ενώσαμε 2 CLA ώστε να έχουμε τα 8 bit που χρειαζόμασταν.

### ADD\_SUB Function

```

32 entity ADD_SUB is
33     Port ( Praxis : in  STD_LOGIC_VECTOR (1 downto 0);
34           Num : in  STD_LOGIC_VECTOR (7 downto 0);
35           F_num : out STD_LOGIC_VECTOR (7 downto 0);
36           Mode : out STD_LOGIC);
37 end ADD_SUB;
38
39 architecture Behavioral of ADD_SUB is
40
41 begin
42
43 process (Praxis,Num)
44 begin
45
46 If (Praxis="00") then F_num<=(Num XOR "00000000");
47                     Mode<='0';
48 elsif (Praxis="01") then F_num<=(Num XOR "11111111");
49                     Mode<='1';
50 elsif (Praxis="10") then F_num<=(Num XOR "11111111");
51                     Mode<='1';
52 else F_num<=(Num XOR "00000000");
53     Mode<='0';
54
55 end if;
56 end process;
57 end Behavioral;

```

### ADDER/SUBER

```

32 entity ADD_SUB_TOP is
33     Port ( Prax : in  STD_LOGIC_VECTOR (1 downto 0);
34           NUM1 : in  STD_LOGIC_VECTOR (7 downto 0);
35           NUM2 : in  STD_LOGIC_VECTOR (7 downto 0);
36           Carry : out STD_LOGIC;
37           Outcomel : out STD_LOGIC_VECTOR (7 downto 0));
38 end ADD_SUB_TOP;
39
40 architecture Structural of ADD_SUB_TOP is
41
42 component Final_CLA is
43     Port ( A_in : in  STD_LOGIC_VECTOR (7 downto 0);
44           B_in : in  STD_LOGIC_VECTOR (7 downto 0);
45           C_in : in  STD_LOGIC;
46           Outcome : out STD_LOGIC_VECTOR (7 downto 0);
47           C_out : out STD_LOGIC);
48 end component;
49
50 component ADD_SUB is
51     Port ( Praxis : in  STD_LOGIC_VECTOR (1 downto 0);
52           Num : in  STD_LOGIC_VECTOR (7 downto 0);
53           F_num : out STD_LOGIC_VECTOR (7 downto 0);
54           Mode : out STD_LOGIC);
55 end component;
56
57 signal data : std_logic_vector(7 downto 0);
58 signal c : std_logic;
59 begin
60
61 CLA : Final_CLA
62     Port map(A_in=>NUM1,
63             B_in=>data,
64             C_in=>c,
65             C_out=>Carry,
66             Outcome=>Outcomel
67             );
68 A_S : ADD_SUB
69     Port map(Praxis=>Prax,
70             Num=>NUM2,
71             F_Num=>data,
72             Mode=>c
73             );
74 end Structural;

```



## REGISTER

```
4 entity Registry is
5   Port ( D : in  STD_LOGIC_VECTOR (7 downto 0);
6         Enable : in  STD_LOGIC;
7         Clk : in  STD_LOGIC;
8         Q : out STD_LOGIC_VECTOR (7 downto 0));
9 end Registry;
10
11 architecture Behavioral of Registry is
12
13   Begin
14
15   Process
16
17   Begin
18
19   Wait until( Clk'EVENT and Clk = '1' );
20   If (Enable = '1') then
21     Q <= D ;
22   End if;
23
24   End process ;
25
26 End Behavioral;
```

## OVF ADDER/SUBER (ανίχνευση)

```
32 entity OVF_CLA is
33   Port ( A : in  STD_LOGIC;
34         B : in  STD_LOGIC;
35         S : in  STD_LOGIC;
36         OVF_out : out STD_LOGIC);
37 end OVF_CLA;
38
39 architecture Behavioral of OVF_CLA is
40
41   begin
42   process(A,B,S)
43   begin
44
45   if(A='0' and B='0' and S='1') then OVF_out<='1';
46   elsif(A='1' and B='1' and S='0') then OVF_out<='1';
47   else OVF_out<='0';
48
49   end if;
50   end process;
51   end Behavioral;
52
```

## FSM\_1

```
34 entity FSM_1 is
35   Port ( CLK : in  STD_LOGIC;
36         Reset : in  STD_LOGIC;
37         BTN0 : in  STD_LOGIC;
38         BTN1 : in  STD_LOGIC;
39         Full_Stack : in  STD_LOGIC;
40         Empty_Stack : in  STD_LOGIC;
41         ovf : in  STD_LOGIC;
42         Mode : in STD_LOGIC_VECTOR(1 downto 0);
43         CounterEnable : out STD_LOGIC;
44         UpDown : out  STD_LOGIC;
45         Output : out  STD_LOGIC_VECTOR(1 downto 0); --praksi
46         CounterRst : out  STD_LOGIC;
47         We : out  STD_LOGIC_VECTOR(0 downto 0);
48         Ovf_Stack : out  STD_LOGIC;
49         Ctrl1 : out  STD_LOGIC;
50         reg1 : out std_logic;
51         reg2 : out std_logic;
52         reg3 : out std_logic);
53 end FSM_1;
54
55 architecture Behavioral of FSM_1 is
56
57   type state_type is (state_0,state_Push,state_Push1,state_Pop,state_Ovf,state_Add,state_Sub,state_USub,state_Change,
58                       state_Add_1,state_Add_2,state_Add_3,state_Add_4,state_Add_5,state_Add_6,state_USub1,state_USub2,state_USub3,
59                       state_Change1,state_Change2,state_Change3,state_Change4,state_Change5,state_Change6,state_Change7,state_Sub_1,
60                       state_Sub_2,state_Sub_3,state_Sub_4,state_Sub_5,state_Sub_6);
61   signal state_next, state: state_type;
```

```

63 begin
64
65 fsm_comb: process(state, state_next, BTN0, BTN1, Empty_Stack, Full_Stack, Mode, ovf)
66 begin
67     case state is
68
69         when state_0=> We<="0";
70             CounterEnable<='0';
71             UpDown<='0';
72             Ctrl<='0';
73             reg1<='0';
74             reg2<='0';
75             reg3<='0';
76             Ovf_Stack<='0';
77             Output<="XX";
78             If (BTN0='1' AND Full_Stack='0' AND Mode="00") then state_next<=state_Push;
79             elsif (BTN1='1' AND Empty_Stack='0' AND Mode="00") then state_next<=state_Pop;
80             elsif (BTN0='1' AND Full_Stack='1' AND Mode="00") then state_next<=state_Ovf;
81             elsif (BTN0='1' AND Mode="01") then state_next<=state_Add;
82             elsif (BTN1='1' AND Mode="01") then state_next<=state_Sub;
83             elsif (BTN0='1' AND Mode="10") then state_next<=state_USub;
84             elsif (BTN1='1' AND Mode="10") then state_next<=state_Change;
85             else state_next<=state_0;
86             end if;
87
88
89         when state_Push1=> state_next<=state_0;
90             CounterEnable<='1';
91             UpDown<='1';
92             Ctrl<='0';
93             reg1<='0';
94             reg2<='0';
95             reg3<='0';
96             Ovf_Stack<='0';
97             We<="0";
98             Ctrl<='0';
99             Output<="XX";
100
101         when state_Push=> state_next<=state_Push1;
102             CounterEnable<='0';
103             UpDown<='1';
104             Ctrl<='0';
105             reg1<='0';
106             reg2<='0';
107             reg3<='0';
108             We<="1";
109             Ctrl<='0';
110             Ovf_Stack<='0';
111             Output<="XX";
112
113         when state_Pop=> state_next<=state_0;
114             CounterEnable<='1';
115             UpDown<='0';

```

```

116         Ctrl<='0';
117         reg1<='0';
118         reg2<='0';
119         reg3<='0';
120         We<="0";
121         Ovf_Stack<='0';
122         Output<="XX";
123
124     when state_Ovf=> Ovf_Stack<='1';
125         We<="0";
126         CounterEnable<='0';
127         UpDown<='0';
128         Ctrl<='0';
129         reg1<='0';
130         reg2<='0';
131         reg3<='0';
132         state_next<=state_Ovf;
133         Output<="XX";
134
135     when state_Add=> We<="0";
136         Ctrl<='0';
137         CounterEnable<='0';
138         UpDown<='0';
139         reg2<='0';
140         reg3<='0';
141         reg1<='1';
142         Ovf_Stack<='0';
143         Output <= "00";
144         state_next<=state_Add_1;
145
146     when state_Add_1=> We<="0";
147         Ctrl<='0';
148         CounterEnable<='1';
149         UpDown<='0';
150         reg1<='0';
151         Ovf_Stack<='0';
152         reg2<='0';
153         reg3<='0';
154         Output <= "00";
155         state_next<=state_Add_2;
156
157     when state_Add_2=> We<="0";
158         Ctrl<='0';
159         CounterEnable<='0';
160         UpDown<='0';
161         reg2<='0';
162         Ovf_Stack<='0';
163         Output <= "00";
164         reg1<='0';
165         reg3<='0';
166         state_next<=state_Add_3;
167
168     when state_Add_3=> We<="0";
169         Ctrl<='0';
170         CounterEnable<='0';
171         UpDown<='0';
172         reg2<='1';
173         reg3<='0';
174         Ovf_Stack<='0';
175         Output <= "00";
176         reg1<='0';
177         state_next<=state_Add_4;
178
179     when state_Add_4=> We<="0";
180         Ctrl<='0';
181         CounterEnable<='0';
182         UpDown<='0';
183         reg2<='0';
184         reg3<='1';
185         Ovf_Stack<='0';
186         Output <= "00";
187         reg1<='0';
188         state_next<=state_Add_5;
189
190     when state_Add_5=> if (ovf='1') then
191         We<="0";
192         CounterEnable<='0';
193         UpDown<='0';

```

```

193         UpDown<='0';
194         Ctrl<='0';
195         reg1<='0';
196         reg2<='0';
197         reg3<='0';
198         Ovf_Stack<='0';
199         Output <= "XX";
200         state_next<=state_0;
201     else
202         We<="1";
203         Ctrl<='1';
204         CounterEnable<='0';
205         UpDown<='0';
206         reg1<='0';
207         reg2<='0';
208         reg3<='1';
209         Ovf_Stack<='0';
210         Output <= "00";
211         state_next<=state_Add_6;
212     end if;
213
214     when state_Add_6=> We<="0";
215         Ctrl<='0';
216         CounterEnable<='1';
217         UpDown<='1';
218         reg1<='0';
219         reg2<='0';
220         reg3<='0';
221         Ovf_Stack<='0';
222         Output <= "00";
223         state_next<=state_0;
224
225     when state_Sub=> We<="0";
226         CounterEnable<='0';
227         UpDown<='0';
228         Ctrl<='0';
229         reg1<='1';
230         Ovf_Stack<='0';
231         Output <= "01";
232         reg2<='0';
233         reg3<='0';
234         state_next<=state_Sub_1;
235
236     when state_Sub_1=> We<="0";
237         Ctrl<='0';
238         CounterEnable<='1';
239         UpDown<='0';
240         reg1<='0';
241         Ovf_Stack<='0';
242         reg2<='0';
243         reg3<='0';
244         Output <= "01";
245         state_next<=state_Sub_2;
246
247     when state_Sub_2=> We<="0";
248         Ctrl<='0';
249         CounterEnable<='0';
250         UpDown<='0';
251         reg2<='0';
252         Ovf_Stack<='0';
253         Output <= "01";
254         reg1<='0';
255         reg3<='0';
256         state_next<=state_Sub_3;
257
258     when state_Sub_3=> We<="0";
259         Ctrl<='0';
260         CounterEnable<='0';
261         UpDown<='0';
262         reg2<='1';
263         reg3<='0';
264         Ovf_Stack<='0';
265         Output <= "01";
266         reg1<='0';
267         state_next<=state_Sub_4;
268
269     when state_Sub_4=> We<="0";
270         Ctrl<='0';

```

```

271         CounterEnable<='0';
272         UpDown<='0';
273         reg2<='0';
274         reg3<='1';
275         Ovf_Stack<='0';
276         Output <= "01";
277         reg1<='0';
278         state_next<=state_Sub_5;
279
280     when state_Sub_5=> if(ovf='1') then
281         We<="0";
282         CounterEnable<='0';
283         UpDown<='0';
284         Ctrl<='0';
285         reg1<='0';
286         reg2<='0';
287         reg3<='0';
288         Ovf_Stack<='0';
289         Output <= "XX";
290         state_next<=state_0;
291     else
292         We<="1";
293         Ctrl<='1';
294         CounterEnable<='0';
295         UpDown<='0';
296         reg1<='0';
297         reg2<='0';
298         reg3<='1';
299         Ovf_Stack<='0';
300         Output <= "01";
301         state_next<=state_Sub_6;
302     end if;
303
304     when state_Sub_6=> We<="0";
305         Ctrl<='0';
306         CounterEnable<='1';
307         UpDown<='1';
308         reg1<='0';
309         reg2<='0';
310         reg3<='0';
311         Ovf_Stack<='0';
312         Output <= "01";
313         state_next<=state_0;
314
315
316
317
318     when state_Usub=> We<="0";
319         CounterEnable<='0';
320         UpDown<='0';
321         Ctrl<='0';
322         reg1<='1';
323         reg2<='1';
324         Ovf_Stack<='0';
325         Output <= "10";
326         reg3<='0';
327         state_next<=state_Usub1;
328
329     when state_Usub1=> We<="0";
330         CounterEnable<='0';
331         UpDown<='0';
332         Ctrl<='0';
333         reg1<='1';
334         reg2<='1';
335         reg3<='1';
336         Ovf_Stack<='0';
337         Output <= "10";
338         state_next<=state_Usub2;
339
340     when state_Usub2=> We<="1";
341         Ctrl<='1';
342         CounterEnable<='0';
343         UpDown<='0';
344         reg1<='0';
345         reg2<='0';
346         reg3<='0';
347         Ovf_Stack<='0';

```

```

348             Output <= "10";
349             state_next<=state_Usub3;
350
351         when state_Usub3=> We<="0";
352             Ctrl1<='0';
353             CounterEnable<='1';
354             UpDown<='1';
355             reg1<='0';
356             reg2<='0';
357             reg3<='0';
358             Ovf_Stack<='0';
359             Output <= "10";
360             state_next<=state_0;
361
362         when state_Change=> We<="0";
363             CounterEnable<='0';
364             UpDown<='0';
365             reg1<='1';
366             reg2<='1';
367             Ovf_Stack<='0';
368             Output <= "11";
369             reg3<='1';
370             Ctrl1<='0';
371             state_next<=state_Change1;
372
373         when state_Change1=>We<="0";
374             CounterEnable<='1';
375             UpDown<='0';
376             reg1<='0';
377             reg2<='0';
378             reg3<='0';
379             Ovf_Stack<='0';
380             Output <= "11";
381             Ctrl1<='0';
382             state_next<=state_Change2;
383
384         when state_Change2=>We<="0";
385             CounterEnable<='0';
386             UpDown<='0';
387             reg1<='0';
388             reg2<='0';
389             reg3<='1';
390             Ovf_Stack<='0';
391             Output <= "11";
392             Ctrl1<='0';
393             state_next<=state_Change3;
394
395         when state_Change3=>We<="0";
396             Ctrl1<='0';
397             CounterEnable<='0';
398             UpDown<='0';
399             reg1<='0';
400             reg2<='1';
401             reg3<='0';
402             Ovf_Stack<='0';
403             Output <= "11";
404             state_next<=state_Change4;
405
406         when state_Change4=>We<="1";
407             Ctrl1<='1';
408             CounterEnable<='0';
409             UpDown<='0';
410             reg1<='0';
411             reg2<='0';
412             reg3<='1';
413             Ovf_Stack<='0';
414             Output <= "11";
415             state_next<=state_Change5;
416
417         when state_Change5=>We<="0";
418             Ctrl1<='0';
419             CounterEnable<='1';
420             UpDown<='1';
421             reg1<='0';
422             reg2<='0';
423             reg3<='0';
424             Ovf_Stack<='0';
425             Output <= "11";

```

```

426             state_next<=state_Change6;
427
428         when state_Change6=>We<="1";
429             Ctrl1<='1';
430             CounterEnable<='0';
431             UpDown<='0';
432             reg1<='0';
433             reg2<='0';
434             reg3<='1';
435             Ovf_Stack<='0';
436             Output <= "11";
437             state_next<=state_Change7;
438
439         when state_Change7=>We<="0";
440             Ctrl1<='0';
441             CounterEnable<='1';
442             UpDown<='1';
443             reg1<='0';
444             reg2<='0';
445             reg3<='0';
446             Ovf_Stack<='0';
447             Output <= "11";
448             state_next<=state_0;
449
450         when others=> state_next<=state_0;
451             Ovf_Stack<='0';
452             We<="0";
453             CounterEnable<='0';
454             UpDown<='0';
455             Ctrl1<='0';
456             reg1<='0';
457             reg2<='0';
458             reg3<='0';
459             Output<="XX";
460
461     end case;
462 end process fsm_comb;
463
464 fsm_synch: process (Reset, CLK)
465 begin
466     if (Reset='1') then state <= state_0;
467         CounterRst<='1';
468     elsif (rising_edge(CLK)) then state <= state_next;
469         CounterRst<='0';
470     end if;
471 end process fsm_synch;
472
473
474 end Behavioral;

```